 


5. Simulate your circuit to ensure that you have done this correctly




6. Create a new Quartus Prime project
 - A. What percentage of FPGA logic resources are used to implement your circuit?

Logic utilization (in ALMs)	13 / 32,070 (< 1 %)
Total registers	8

- B. What is the maximum clock frequency, F_{max} , at which your circuit can be operated?

Slow 1100mV 85C Model				
	Fmax	Restricted Fmax	Clock Name	Note
1	643.09 MHz	621.89 MHz	KEY[0]	limit due to low minimum...e width violation (tcl)


7. Use the Quartus Prime RTL Viewer to see how the Quartus Prime software synthesized your circuit. there are two more HEX blocks.

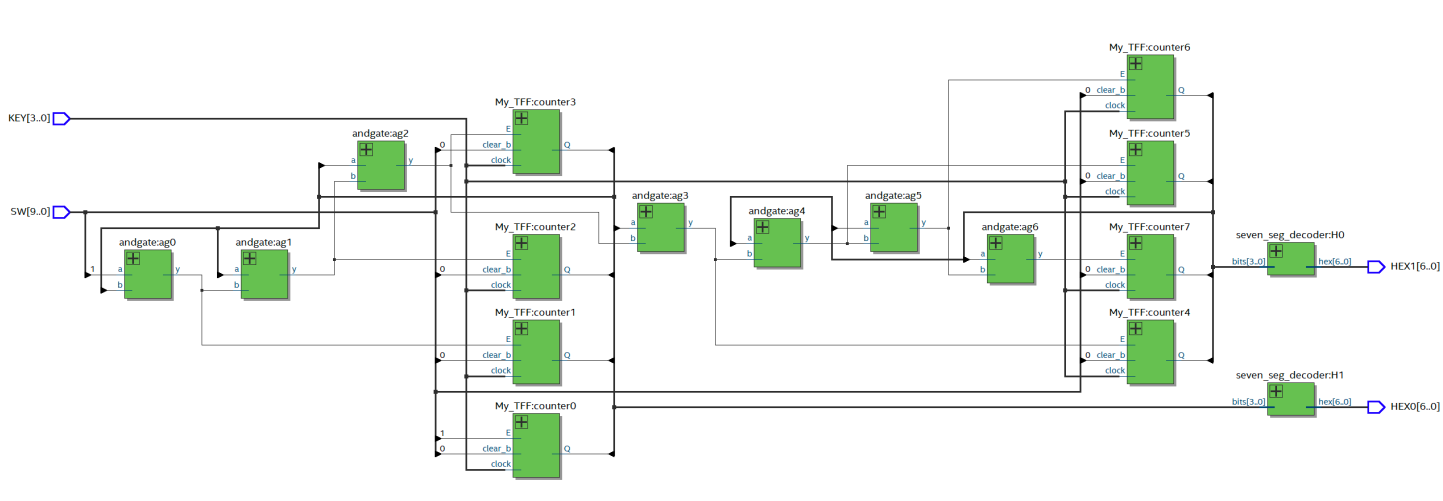


Prat II

- A. The check for the maximum value is not necessary in the example above. Why?
when $4'b1111 + 1'b1$, it will be $5'b10000$, but there is only 4 bits, therefore, the value will become $4'b0000$ which is 0.
- B. If you wanted this 4-bit counter to count from 0-9, what would you change?
if $(q == 4'b1111)$ should change to if $(q == 4'b1001)$
- C. At this speed, what do you expect to see on the display?
I cannot see the number clearly.

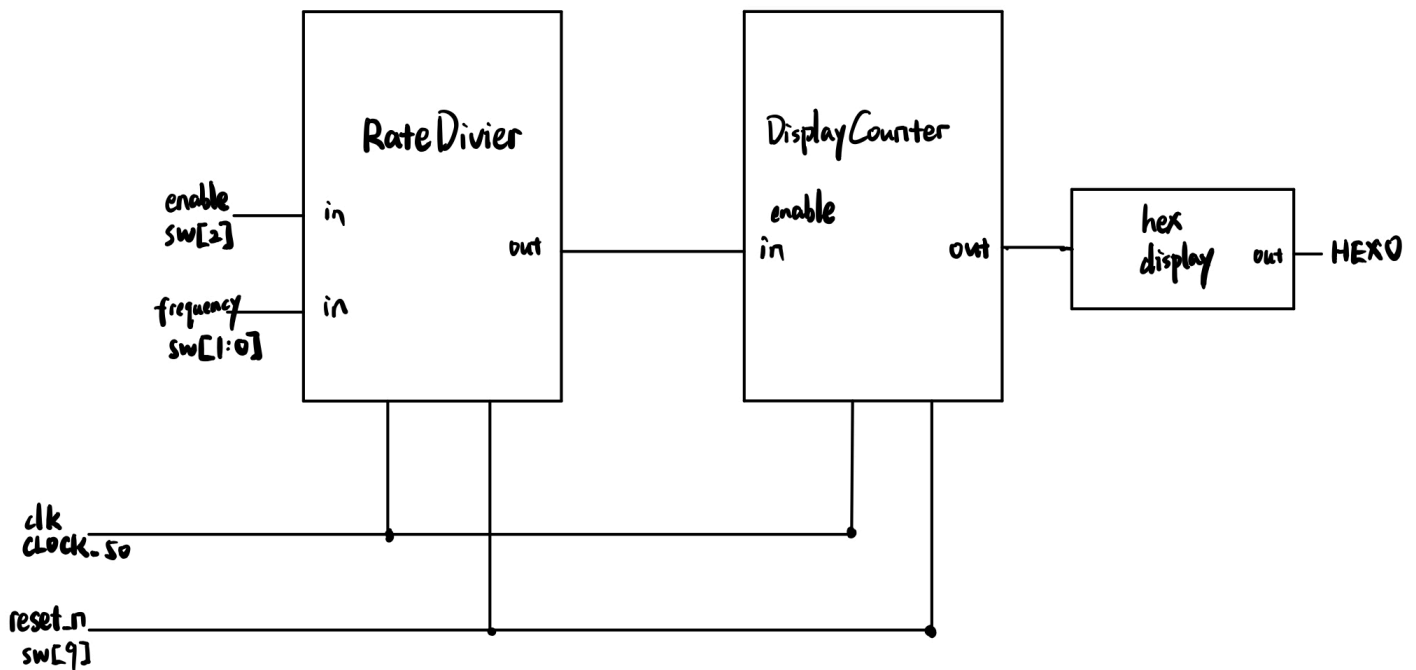- D. How large a counter is required to count 50 million clock cycles?
combine two counters to one counter
- E. How many bits would you need to represent such a value?
28bits
1. Draw a schematic of the circuit you wish to build.



2. Write a Verilog module that realizes the behaviour described in your schematic.
see the ClockCounter.v file
3. Simulate your circuit with ModelSim for a variety of input settings

 


Prat III

1. Morse Pattern Representation with fixed bit-bit-width

Letter	Morse Code	Pattern Representation (pattern length is <u>14</u> bits)
S	• • •	10101000000000
T	—	11000000000000
U	• • —	10101100000000
V	• • • —	10101011000000
W	• — —	10111011000000
X	— • • —	111010101110
Y	— • — —	1110101110110
Z	— — • •	111011101000

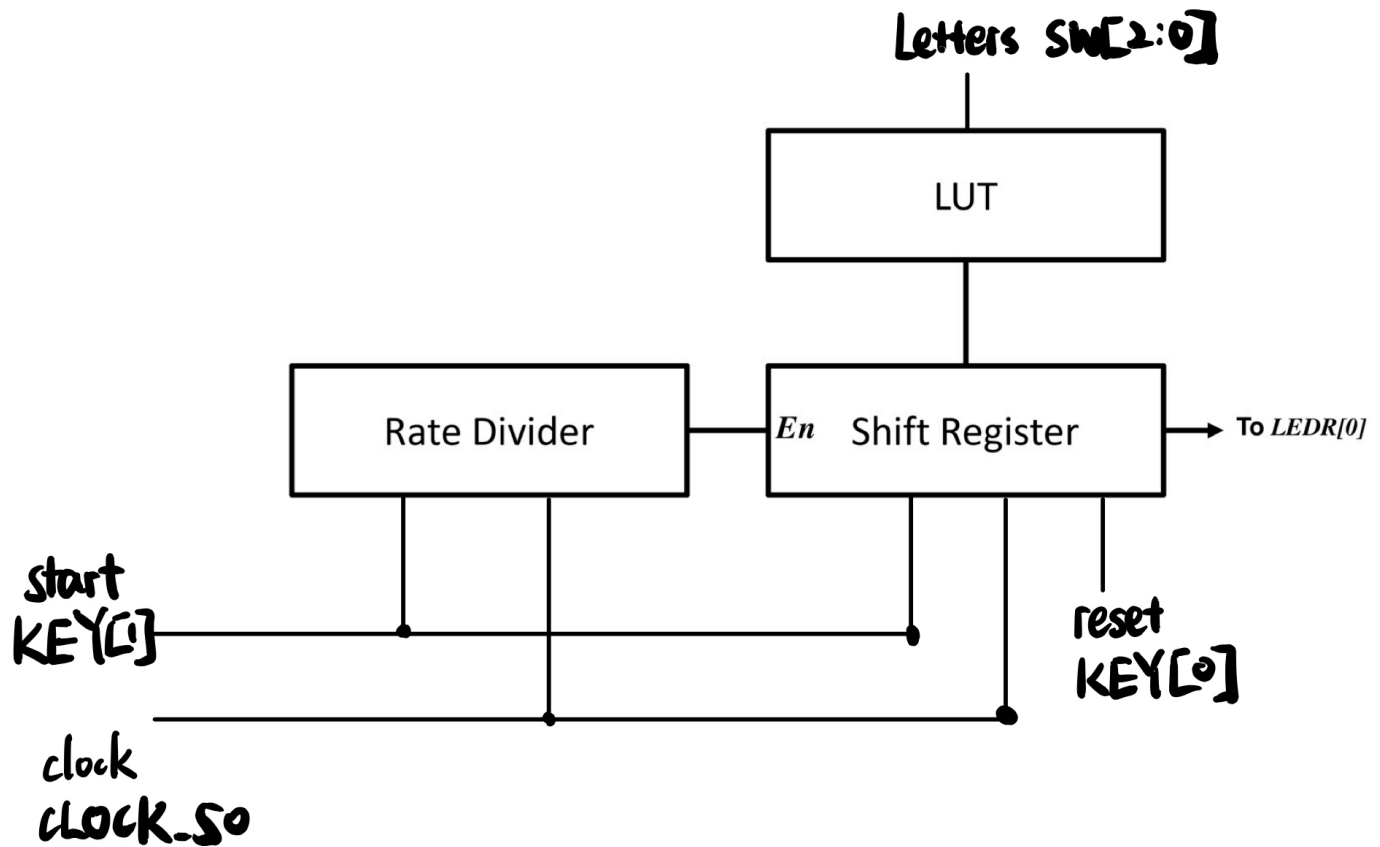2. Design your circuit by first drawing a schematic of the circuit.



3. Write a Verilog module that realizes the behaviour described in your schematic
see the MorseCoder.v file