


# CSC258 Lab1 Pre-lab Report

## Building Circuits using 7400-Series Chips

Yuchen Fan  
1003800265

Part I  $f = xs' + ys$

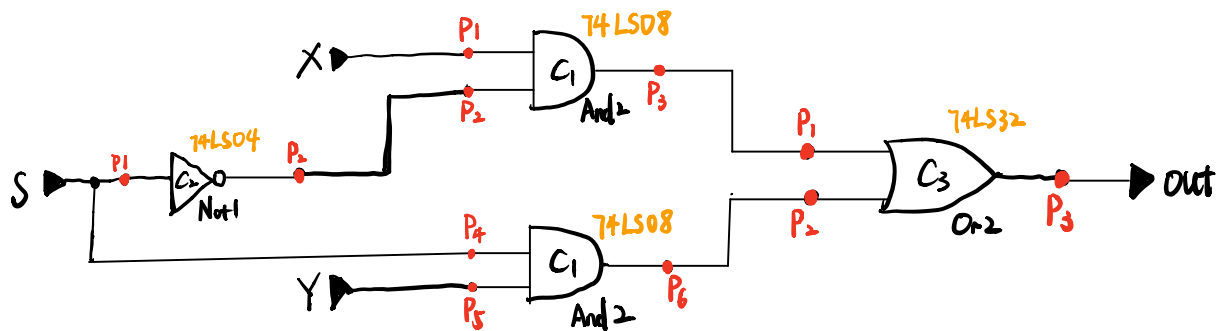Draw circuit and truth table for the above function, indicate pin numbers on the chips, specify which chip was used for which gate and which pins the inputs and outputs are connected to.



Chips used

C1 - 74LS08

C2 - 74LS04

C3 - 74LS32

Connected to all chips

PIN#7 - Gnd

PIN#14 - Vcc


Truth table

S	X	Y	Out
1	1	1	1
0	1	1	1
1	0	1	1
0	0	1	0
1	1	0	0
0	1	0	1
1	0	0	0
0	0	0	0
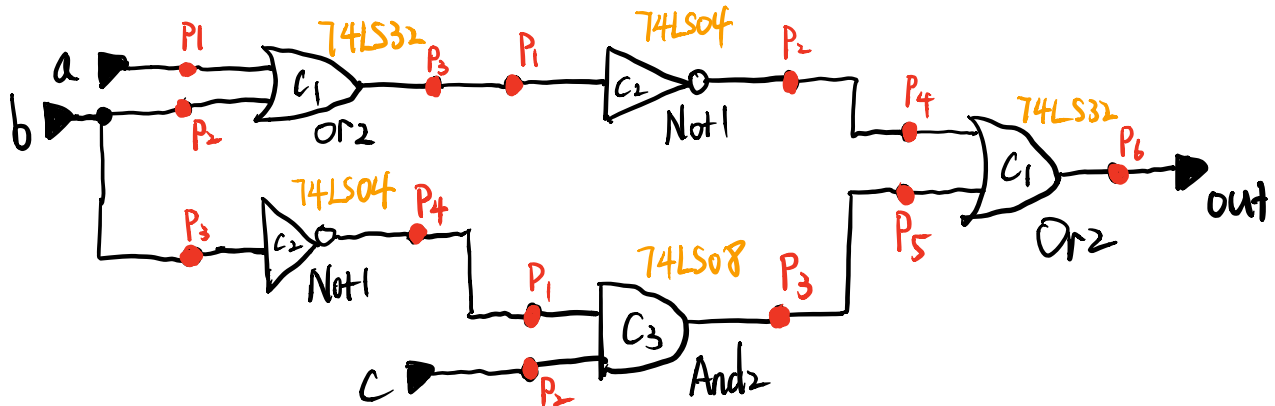
## Part II

$$f = (a+b)' + cb'$$

Draw circuit and truth table for the above function, indicate pin numbers on the chips, specify which chip was used for which gate and which pins the inputs and outputs are connected to.



Chips used

C1 -74LS32

C2 -74LS04

C3 -74LS08

Connected to all chips

PIN#7 - Gnd

PIN#14 -Vcc

Truth table

a	b	c	$(a+b)'$	$cb'$	out
1	1	1	0	0	0
0	1	1	0	0	0
1	0	1	0	1	1
0	0	1	1	1	1
1	1	0	0	0	0
0	1	0	0	0	0
1	0	0	0	0	0
0	0	0	1	0	1

Find whether there is a cheaper implementation for the design

Yes,

$$(a+b)' \Leftrightarrow a'b'$$

$$a'b' + cb' \Leftrightarrow (a'+c)b'$$

we only use two NOT gates, one AND gate and one OR gate.