

CSC258 Lab #6 Pre-Lab

Finite State Machines

Last name: Fan

First name: Yuchen


Student number: 1003800265

Prat I

1. Complete sequence_detector.v
see the file sequence_detector.v
2. is the resetn signal is an synchronous or asynchronous reset?
reset is synchronous and active low.
if I want to reset the state, I need to make sure the clock is on when the reset is enabled.
3. Complete the state table

Present state	Input	Next state	Output
A:000	0	A:000	0
A:000	1	B:001	0
B:001	0	A:000	0
B:001	1	C:010	0
C:010	0	E:100	0
C:010	1	D:011	0
D:011	0	E:110	0
D:011	1	F:101	0
E:100	0	A:000	0
E:100	1	G:110	0
F:101	0	E:100	1
F:101	1	F:101	1
G:110	0	A:000	1
G:110	1	C:010	1

4. Simulate your circuit using ModelSim
see the file sequence_detector.do

 



Prat II

1. understand the circuitry
2. draw a table that shows the state of the Registers and control signals for each cycle of your computation

Cycle	Computation	ld_a	ld_b	ld_alu_out	ld_r	alu_select_a	alu_select_b	A	B	R
0	$A * X$	1	0	1	0	2'b00	2'b11	$A * X$	B	
1	$AX + B$	0	1	1	0	2'b00	2'b01	$A * X$	$AX + B$	
2	$X(AX+B)$	0	1	1	0	2'b11	2'b01	$A * X$	$X(AX+B)$	
3	$X(AX+B)+C$	0	0	0	1	2'b01	2'b10	$A * X$	$X(AX+B)$	$X(AX+B)+C$

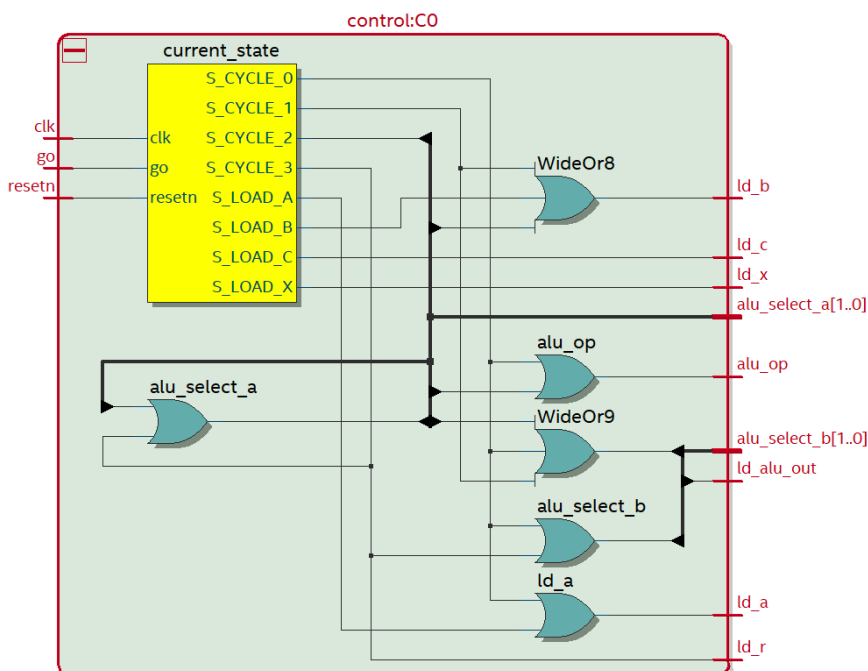3. Draw a state diagram for your controller
see the next page
4. Modify the controller part
see the file poly_function.v
5. examine the circuit



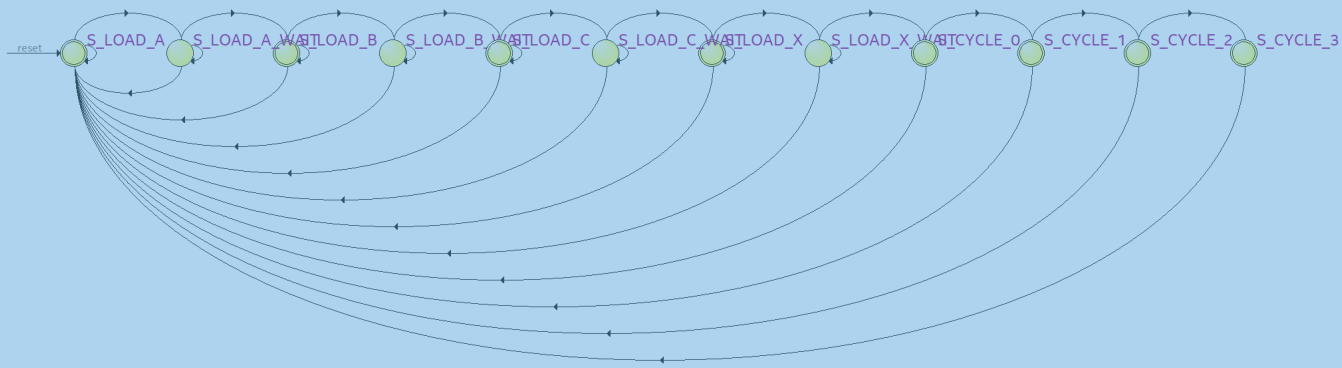

6. Simulate your circuit with ModelSim

