

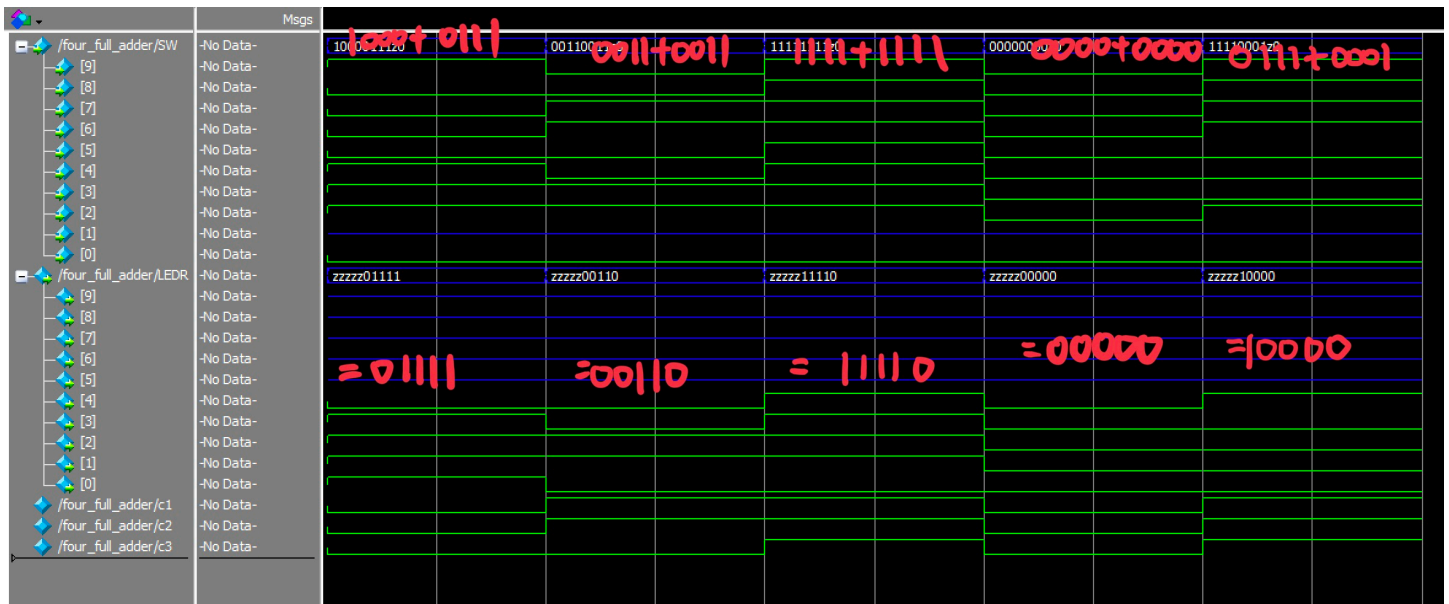


1. Draw a schematic showing your code structure

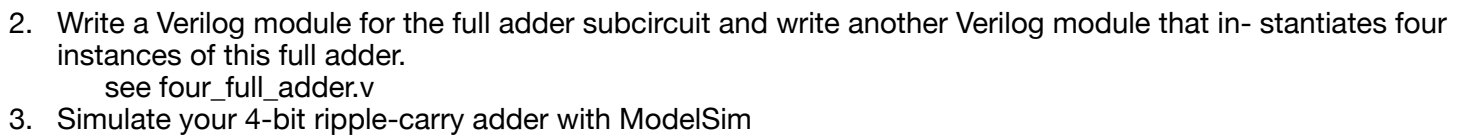

Part III

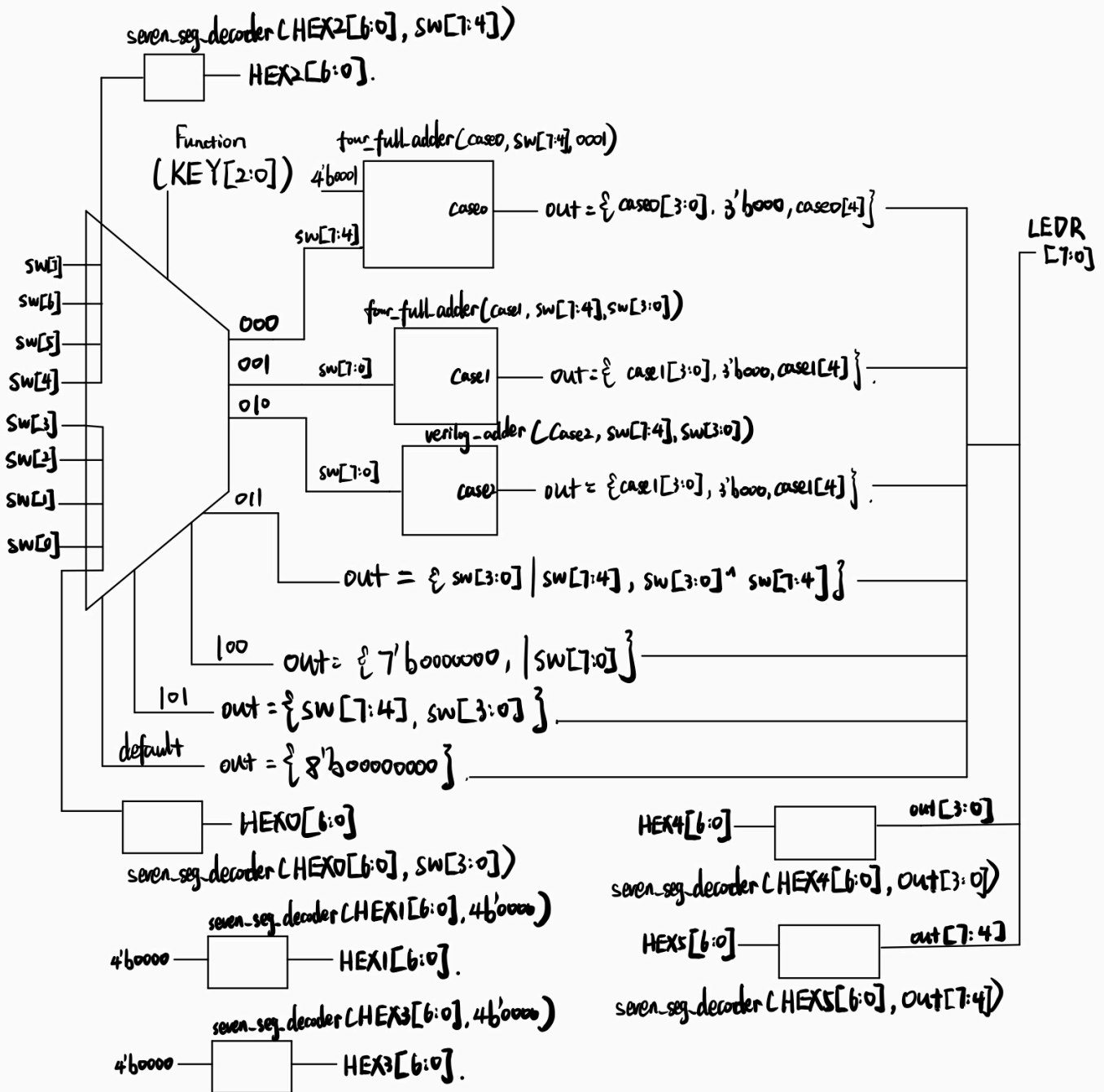1. Draw a schematic showing your code structure



2. Write a Verilog module for the ALU including all inputs and outputs
see ALU.v
3. Simulate your circuit with ModelSim

